

Solution. Applying Kirchoff's second law to the closed network $ABDA$ (Fig. 6.10),

$$5I + 40I_g - 5[0.2 - I] = 0$$

$$10I + 40I_g = 1 \quad \dots(1)$$

or For the network $BDCB$,

$$40I_g + 5.2(0.2 - I + I_g) - 5(I - I_g) = 0$$

$$50.2I_g - 10.2I = -1.04 \quad \dots(2)$$

$$I_g = -\frac{0.2}{910} = -0.0002198 \text{ A.}$$

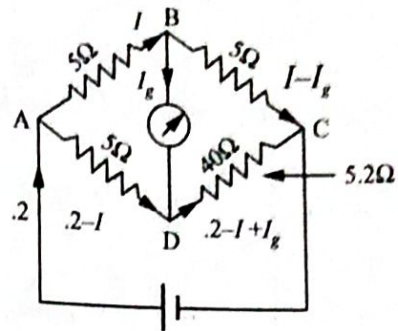


FIG. 6.10

ELECTRICAL MEASUREMENTS

6.7 CAREY FOSTER BRIDGE

Description. The Carey Foster bridge is a form of Wheatstone's bridge. It consists of a uniform wire AB of length 1 metre stretched on a wooden board (Fig. 6.11).

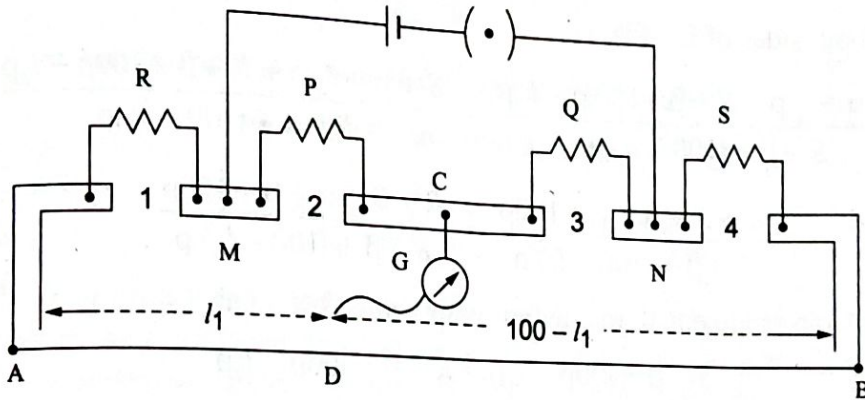


FIG. 6.11

Two equal resistances P and Q are connected in gaps 2 and 3. The unknown resistance R is connected in gap 1. A standard resistance S , of the same order of resistance as R , is connected in gap 4. A Leclanche cell is connected across MN . A galvanometer G is connected between the terminal C and a sliding contact maker D .

Theory. The contact maker is moved until the bridge is balanced. Let l_1 be the balancing length as measured from end A . Let α and β be the end resistances at A and B . Let ρ be the resistance per unit length of the wire.

From the principle of Wheatstone's bridge,

$$\frac{P}{Q} = \frac{R + \alpha + l_1\rho}{S + \beta + (100 - l_1)\rho} \quad \dots(1)$$

The resistances R and S are interchanged and the bridge is again balanced. The balancing length l_2 is determined from the same end A . Then,

$$\frac{P}{Q} = \frac{S + \alpha + l_2\rho}{R + \beta + (100 - l_2)\rho} \quad \dots(2)$$

Figs. 6.12 and 6.13 represent the equivalent Wheatstone's bridge circuit in the two cases.

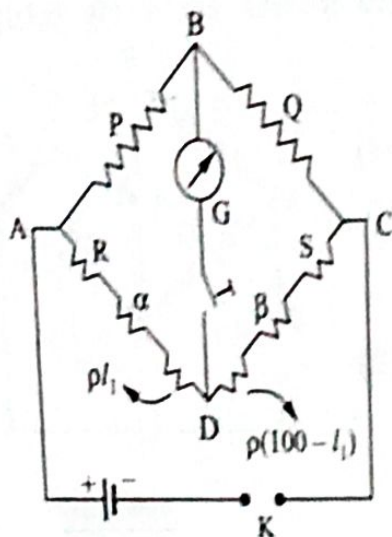


FIG. 6.12

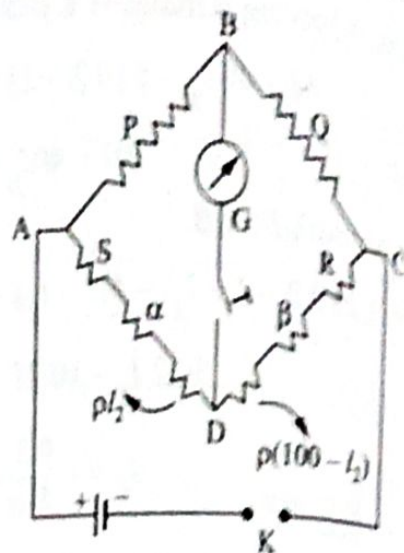


FIG. 6.13

From Eqns. (1) and (2),

$$\frac{R + \alpha + l_1 \rho}{S + \beta + (100 - l_1) \rho} = \frac{S + \alpha + l_2 \rho}{R + \beta + (100 - l_2) \rho} \quad \dots(3)$$

Adding 1 to both sides of Eq. (3),

$$\frac{R + \alpha + l_1 \rho + S + \beta + 100 \rho - l_1 \rho}{S + \beta + (100 - l_1) \rho} = \frac{S + \alpha + l_2 \rho + R + \beta + 100 \rho - l_2 \rho}{R + \beta + (100 - l_2) \rho}$$

$$\therefore \frac{R + S + \alpha + \beta + 100 \rho}{S + \beta + (100 - l_1) \rho} = \frac{R + S + \alpha + \beta + 100 \rho}{R + \beta + (100 - l_2) \rho}$$

Since the numerators are equal, the denominators must be equal.

$$\therefore S + \beta + 100 \rho - l_1 \rho = R + \beta + 100 \rho - l_2 \rho \quad \dots(4)$$

$$\text{or } S - l_1 \rho = R - l_2 \rho$$

$$\therefore R = S + \rho (l_2 - l_1) \quad \dots(5)$$

To find ρ . A standard resistance of 0.1Ω is connected in gap 1. A thick copper strip is connected in gap 4 i.e., $R = 0.1 \Omega$ and $S = 0$. The balancing length l_1' is determined. The standard resistance and the thick copper strip are interchanged. The balancing length l_2' is determined.

$$\text{From Eq. (5), } 0.1 = S + \rho (l_2' - l_1')$$

$$\text{or } \rho = \frac{0.1}{(l_2' - l_1')}$$

Thus by knowing S and ρ , the unknown resistance R is calculated.

Determination of Resistivity

The resistance R of the given wire is determined using Carey Foster's Bridge. The length of the wire L is measured. The mean radius (r) of the wire is found with a screw gauge. Then, the resistivity of the material of the wire is calculated using the formula,

$$s = \frac{\pi r^2 R}{L} \text{ ohm-metre.}$$

Determination of the temperature coefficient of resistance

Let R_0 and R_t be the resistances of a wire at temperatures 0°C and $t^\circ\text{C}$. Then,

$$R_t = R_0(1 + \alpha t)$$

or

$$\alpha = \frac{R_t - R_0}{R_0 t} = \frac{1}{R_0} \frac{dR}{dt}$$

where α is the temperature coefficient of resistance of the material.

The increase of resistance per unit temperature coefficient of resistance.

The given wire is wound non-inductively in the form of a double spiral on a glass tube. It is immersed in a beaker containing ice at 0°C . The resistance of the wire is determined as above. The resistance of the wire is determined at $10^\circ, 20^\circ, 30^\circ, \dots, 100^\circ\text{C}$. A graph is drawn with temperature along the X-axis and resistance along the Y-axis (Fig. 6.14). A straight line is obtained.

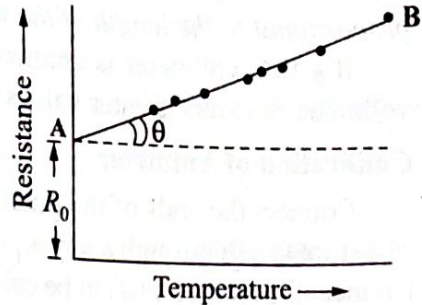


FIG. 6.14

$$\left. \begin{array}{l} \text{Slope of} \\ \text{the line} \end{array} \right\} = \tan \theta = \frac{dR}{dt}$$

$$Y \text{ intercept} = R_0$$

α is calculated using the formula, $\alpha = \frac{1}{R_0} \frac{dR}{dt}$

Note. Let R_1 and R_2 be the resistances at $t_1^\circ\text{C}$ and $t_2^\circ\text{C}$ respectively.

$$R_1 = R_0 [1 + \alpha t_1] \text{ and } R_2 = R_0 [1 + \alpha t_2]$$

$$\therefore \alpha = \frac{R_2 - R_1}{R_1 t_2 - R_2 t_1}$$

Example 1. In an experiment with Carey Foster bridge, the shift in the balance point is 5.4 cm when a thick copper strip and one ohm resistance are interchanged. The one ohm resistance is then replaced by an unknown resistance. Now the balance point shifts by 10 cm on interchanging. Calculate the unknown resistance.

Solution.

$$\rho = \frac{1}{5.4} \text{ ohm/cm}$$

$$R = S + \rho(l_2 - l_1) = 0 + \frac{1}{5.4} \times 10 = 1.85 \text{ ohm.}$$

6.8 POTENTIOMETER

Principle. A potentiometer is a device for measuring or comparing potential differences. A potentiometer can be used to measure any electrical quantity which can be converted into a proportionate D.C potential difference.

It consists of a uniform wire AB of length 10 m stretched on a wooden board (Fig. 6.15). A steady current is passed through the wire AB with the help of a cell of EMF E . Let

ρ = resistance per unit length of potentiometer wire, and

I = steady current passing through the wire.

Let C be a variable point.

Let $AB = L$ and $AC = l$.

PD across $AB = L\rho I$,

and

PD across $AC = l\rho I$

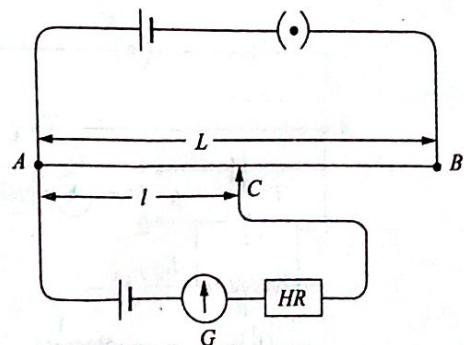


FIG. 6.15

$$\frac{PD \text{ across } AB}{PD \text{ across } AC} = \frac{L\rho l}{l\rho l} = \frac{L}{l}$$

$$\therefore PD \text{ across } AC = \frac{l}{L} \times PD \text{ across } AB$$

i.e., for a steady current passing through the potentiometer wire AB, the PD across any length is proportional to the length of the wire.

If a D.C voltmeter is connected between A and the variable point C, it will be noted that the voltmeter registers greater values of PD's as the point C slides from A to B.

Calibration of Ammeter

Connect the ends of the potentiometer wire to the terminals of a storage cell through a key K_1 (Fig. 6.16). S is a standard cell. Connect the ammeter (A) to be calibrated in series with a battery, key K_2 , a rheostat and a standard resistance R . When a current I passes through the standard resistance R , the PD across R is IR . This potential drop is measured with the help of potentiometer.

Connect 1 and 3 and balance the EMF of the standard cell against the potentiometer. Find the balancing length (l) from A. The PD per cm of the potentiometer = E/l .

Connect 2 and 3. Adjust the rheostat so that the ammeter reads a value A_1 . Balance the PD across R against the potentiometer and find the balancing length l_1 .

$$PD \text{ across } R = El_1/l$$

$$\text{Current through } R = El_1/(IR)$$

$$\text{Correction to ammeter reading} = (El_1/IR) - A_1$$

Similarly, the corrections for other ammeter readings are determined. A calibration curve is plotted for ammeter, taking ammeter readings on X-axis and corrections on Y-axis (Fig. 6.17).

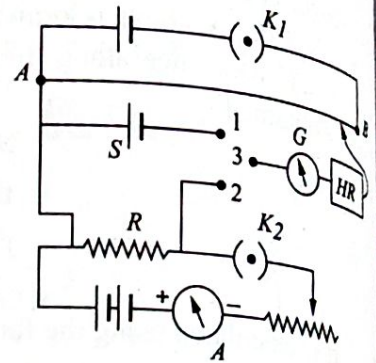


FIG. 6.16

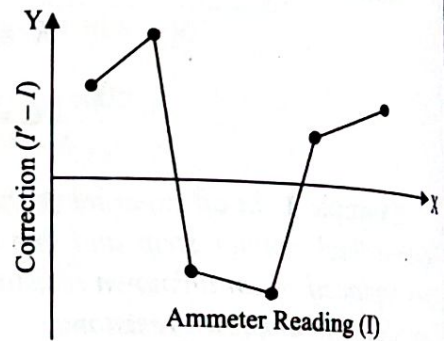


FIG. 6.17

Calibration of Voltmeter (Low range)

The connections are made as shown in Fig. 6.18. The voltmeter is connected parallel to R . Let l be the balancing length for the standard cell. The PD across R is balanced against the potentiometer. Let l_1 be the balancing length when the voltmeter reads V_1 .

$$PD \text{ across } R = El_1/l$$

$$\text{Correction to voltmeter} = (El_1/l) - V_1$$

The experiment is repeated for various readings of the voltmeter and a calibration graph is drawn (Fig. 6.19).

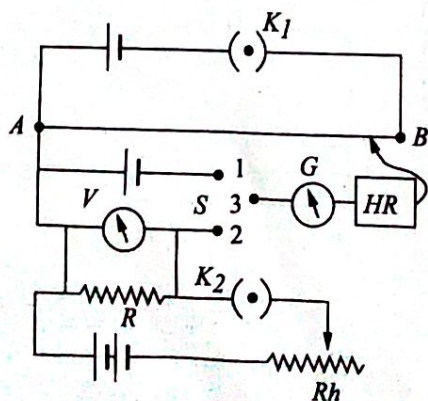


FIG. 6.18

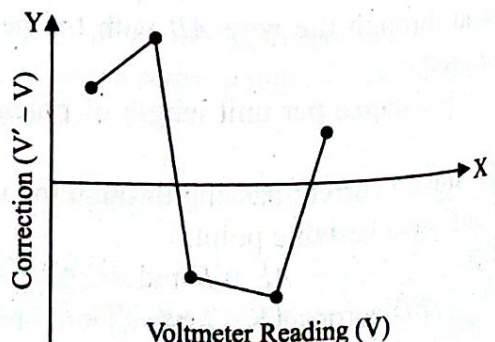


FIG. 6.19

Calibration of voltmeter (High range)

Connections are made as shown in Fig. 6.20. Take suitable high resistances in P and Q such that the PD across P does not exceed the PD across the potentiometer. The balancing length l for the standard cell is determined first. Then the PD across P is balanced against the potentiometer and the balancing length l_1 is determined.

$$\text{PD across } P = El_1/l$$

$$\text{PD across } P + Q = \left(\frac{P+Q}{P}\right)\left(\frac{El_1}{l}\right)$$

$$\text{Correction to voltmeter} = \left(\frac{P+Q}{P}\right)\left(\frac{El_1}{l}\right) - V_1$$

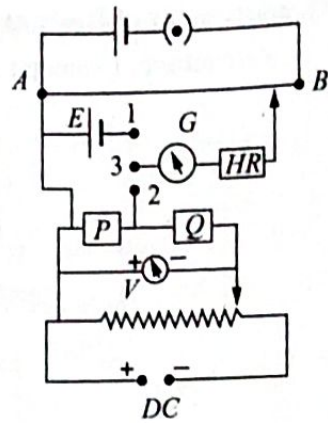


FIG. 6.20

The experiment is repeated for various readings of the voltmeter. A calibration curve is plotted for voltmeter, taking voltmeter readings on X -axis and corrections on Y -axis.

Determination of the Internal Resistance of a cell

Circuit Diagram. AB is the potentiometer wire (Fig. 6.21). A steady current is passed through the wire with the help of a battery. E is the cell whose internal resistance is to be measured. A resistance box R is connected across the cell through a key K_2 .

Procedure: Closing key K_1 , a balancing point is obtained on the potentiometer wire with K_2 open. The balancing length $l_1 (= AC)$ now is a measure of the EMF E of the cell.

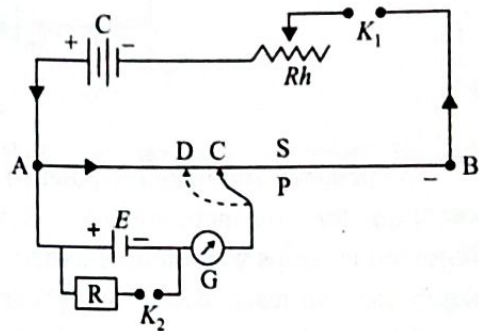


FIG. 6.21

$$E \propto l_1 \quad \dots(1)$$

The key K_2 is closed. A resistance R is introduced in the box. Without disturbing rheostat Rh , the balancing length $l_2 (= AD)$ is measured. This is a measure of the PD V of the cell. Then

$$V \propto l_2 \quad \dots(2)$$

From Eqns. (1) and (2),

$$\frac{E}{V} = \frac{l_1}{l_2} \quad \dots(3)$$

Let E be the EMF of the cell and r the internal resistance. Let V be the PD across the cell when supplying a current I through the external resistance R .

Then,
$$V = IR \quad \dots(4)$$

and
$$E = I(R + r) \quad \dots(5)$$

\therefore
$$\frac{E}{V} = \frac{R+r}{R} = 1 + \frac{r}{R} \quad \dots(6)$$

Comparing Eqns. (3) and (6),

$$1 + \frac{r}{R} = \frac{l_1}{l_2}$$

\therefore
$$r = \left(\frac{l_1 - l_2}{l_2}\right)R \quad \dots(7)$$

Hence r is calculated.

Measurement of Resistance of a coil with a Potentiometer

Procedure: Connections are made as shown in Fig. 6.22.

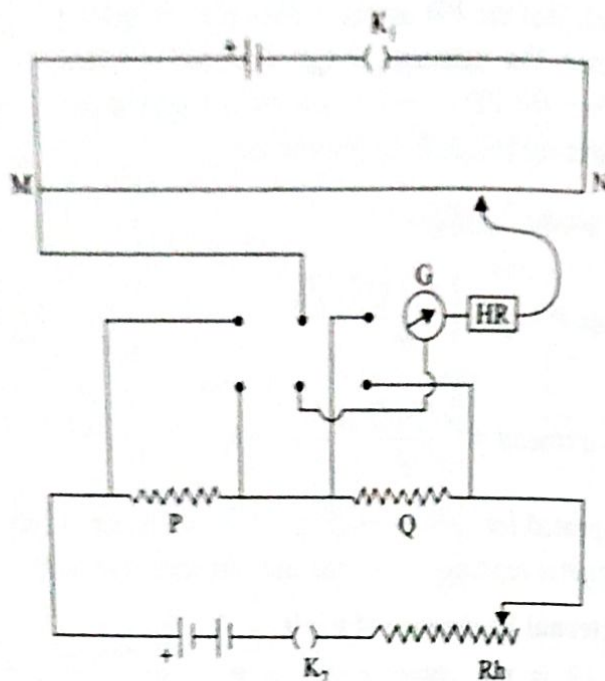


FIG. 6.22

The positive and negative poles of a storage battery are connected to the ends M and N of the potentiometer wire including a key K_1 in the circuit. The two resistances P and Q to be compared are joined in series with another battery, a rheostat and a plug key K_2 . By means of the double throw switch, the two resistances P and Q can be successively included in the galvanometer circuit. Care should be taken to see that the high potential terminals of the resistances P and Q are connected to the high potential terminal M of the potentiometer wire.

- (i) The P.D across the resistance P is first balanced on the potentiometer. The balancing length l_1 is found out.
- (ii) Keeping the current passing through P and Q unaltered, the P.D across Q is balanced on the potentiometer wire. The balancing length in this case l_2 is found out.

Theory: Let i be the current passing through the resistances P and Q . The potential differences across P and Q are iP and iQ respectively.

Now $iP \propto l_1$ and $iQ \propto l_2$.

By division,

$$\frac{P}{Q} = \frac{l_1}{l_2}$$

The experiment is repeated by altering the current passing through the resistances by means of the rheostat. The mean value of the ratio between the resistances is determined.

If one of the resistances is known, the value of the other resistance can be found out.

$$Q = P \left(\frac{l_2}{l_1} \right)$$

Determination of Resistivity

The length of the wire L is measured.

The mean radius (r) of the wire is found with a screw gauge.

The resistivity of the material of the wire is calculated using the formula,

$$s = Q \left(\frac{\pi r^2}{L} \right) \Omega m.$$

8.1 SEEBECK EFFECT

When two dissimilar metal wires are joined together so as to form a closed circuit and if the two junctions are maintained at different temperatures, an emf is developed in the circuit (Fig. 8.1). This causes a current to flow in the circuit as indicated by the deflection in the galvanometer G . This phenomenon is called the *Seebeck effect*.

This arrangement is called a *thermocouple*. The emf developed is called *thermo emf*. The thermo emf so developed depends on the temperature difference between the two junctions and the metals chosen for the couple. Seebeck arranged the metals in a series as follows:

Bi, Ni, Pd, Pt, Cu, Mn, Hg, Pb, Sn, Au, Ag, Zn, Cd, Fe, Sb.

When a thermocouple is formed between any two of them, the thermoelectric current flows through the hot junction from the metal occurring earlier to the metal occurring later in the list. The more removed are the two metals in the list, the greater is the thermo emf developed. The metals to the left of Pb are called *thermoelectrically negative* and those to its right are *thermoelectrically positive*.

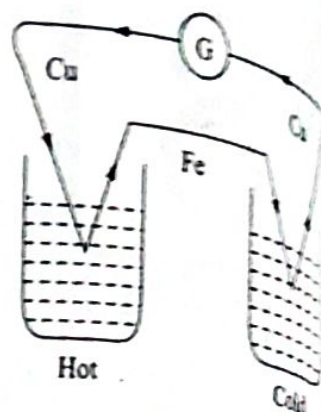


FIG. 8.1

8.2 LAWS OF THERMO e.m.f.

(i) **Law of Intermediate Metals.** The introduction of any additional metal into any thermoelectric circuit does not alter the thermo emf provided the metal introduced is entirely at the same temperature as the point at which the metal is introduced.

If ${}_aE_b$ is the emf for a couple made of metals A and B , and ${}_bE_c$ that for the couple of metals B and C , then the emf for couple of metals A and C is given by

$${}_aE_c = {}_aE_b + {}_bE_c$$

(ii) **Law of Intermediate Temperatures.** The thermo emf E_1^3 of a thermocouple whose junctions are maintained at temperatures T_1 and T_3 is equal to the sum of the emfs E_1^2 and E_2^3 when the junctions are maintained at temperatures T_1, T_2 and T_2, T_3 , respectively. Thus

$$E_1^3 = E_1^2 + E_2^3$$

8.3 MEASUREMENT OF THERMO EMF USING POTENTIOMETER

Thermo emfs are very small, of the order of only a few millivolts. Such small emfs are measured using a potentiometer. A ten-wire potentiometer of resistance R is connected in series with an accumulator and resistance boxes P and Q (Fig. 8.2). A standard cell of emf E is connected in the secondary circuit. The positive terminal of the cell is, connected to the positive of Q . The negative terminal of the cell is connected to a galvanometer and through a key to the negative of Q .

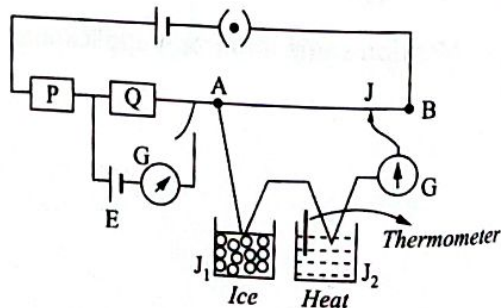


FIG. 8.2

A resistance of $100 ER$ ohms is taken in Q . The resistance in P is adjusted so that on closing the key, there is no deflection in the galvanometer. Now, the PD across $100 ER$ ohms is equal to E .

$$\left. \begin{array}{l} \text{PD across } R \text{ ohms} \\ \text{of the potentiometer} \end{array} \right\} = \frac{ER}{100 ER} \text{ volt} = \frac{1}{100} \text{ volt} = 10 \text{ millivolt.}$$

Thus the fall of potential per metre of the potentiometer wire is 1 millivolt. So we can measure thermo emf up to 10 millivolt.

Without altering the resistances in P and Q , the positive of the thermocouple is connected to the positive terminal of the potentiometer and the negative of the thermocouple to a galvanometer and jockey. One junction is kept in melting ice and the other junction in an oil bath or in a sand bath. The jockey is moved till a balance is obtained against the small emf e of the thermocouple. Let $l = 1$ cm be the balancing length. Then,

$$\text{thermo emf } e = \frac{1}{100} \text{ millivolt.}$$

Keeping the cold junction at 0°C , the hot junction is heated to different temperatures. The thermo emf generated is determined for different temperatures of the hot junction. A graph is drawn between thermo emf and the temperature of the hot junction (Fig. 8.3). The graph is a parabolic curve.

The thermo emf E varies with temperature according to $E = at + bt^2$, where a and b are constants. The thermo emf increases as the temperature of the hot junction increases, reaches a maximum value T_n , then decreases to zero at a particular temperature T_i . On further increasing the difference of temperature, emf is reversed in direction.

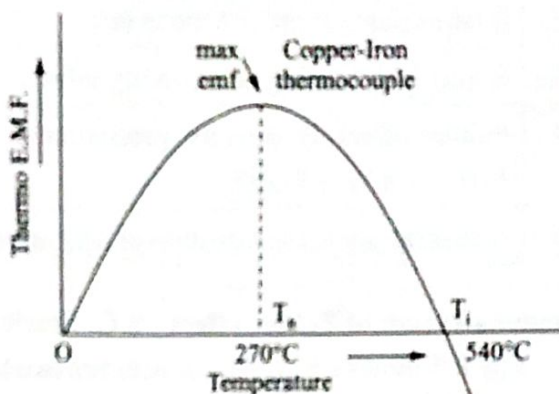


FIG. 8.3

For a given temperature of the cold junction, the temperature of the hot junction for which the thermo emf becomes maximum is called the neutral temperature (T_n) for the given thermocouple.

For a given temperature of the cold junction, the temperature of the hot junction for which the thermo emf becomes zero and changes its direction is called the inversion temperature (T_i) for the given thermocouple.

T_n is a constant for the pair of metals. T_i is variable. T_i is as much above the neutral temperature as the cold junction is below it.

8.4 PELTIER EFFECT

Consider a copper-iron thermocouple (Fig. 8.4). When a current is allowed to pass through the thermocouple in the direction of arrows (from A to B), heat is absorbed at the junction B and generated at the junction A . This absorption or evolution of heat at a junction when a current is sent through a thermocouple is called Peltier effect. The Peltier effect is a reversible phenomenon. If the direction of the current is reversed, then there will be cooling at the junction A and heating at the junction B .

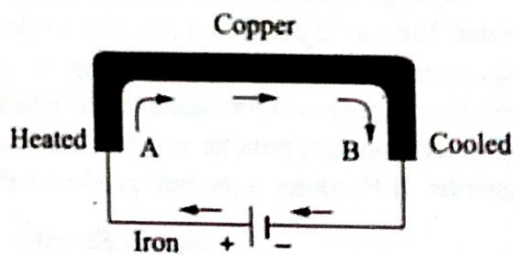


FIG. 8.4

When an electric current is passed through a closed circuit made up of two different metals, one junction is heated and the other junction is cooled. This is known as Peltier effect.

The amount of heat H absorbed or evolved at a junction is proportional to the charge q passing through the junction, i.e.,

$$H \propto q \quad \text{or} \quad H \propto It$$

or

$$H = \pi It$$

where π is a constant called Peltier coefficient.

When $I = 1\text{A}$ and $t = 1\text{s}$, then $H = \pi$.

The energy that is liberated or absorbed at a junction between two dissimilar metals due to the passage of unit quantity of electricity is called Peltier coefficient.

It is expressed in joule/coulomb i.e., volt. The Peltier coefficient is not constant but depends on the temperature of the junction.

The Peltier effect is different from the I^2R Joule heating effect. The main differences are given below.

	Peltier Effect	Joule Effect
1.	It is a reversible effect.	It is an irreversible effect.
2.	It takes place at the junctions only.	It is observed throughout the conductor.
3.	It may be a heating or a cooling effect.	It is always a heating effect.
4.	Peltier effect is directly proportional to I ($H = \pm \pi It$)	Amount of heat evolved is directly proportional to the square of the current.
5.	It depends upon the direction of the current.	It is independent of the direction of the current.

Demonstration of Peltier effect - S.G. Starling Method.

Fig. 8.5 shows a bismuth bar between two bars of antimony. Two coils C_1 and C_2 of insulated copper wire are wound over the two junctions J_1 and J_2 . These coils are connected across the two gaps of a metre-bridge and the balance-point is found on the bridge wire. Now a current is passed through the rods from Sb to Bi . The junction J_1 is heated and J_2 is cooled. The resistance of copper varies rapidly with change of temperature. Hence the balance in the bridge is immediately upset. The galvanometer shows a deflection. If the current is reversed, the deflection in the galvanometer also gets reversed. This shows that the junction J_1 is now cooled and J_2 is heated.

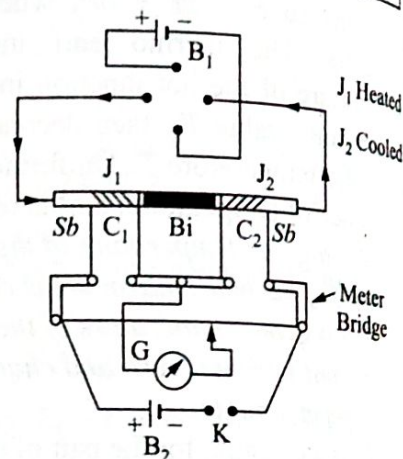


FIG. 8.5

Determination of the Peltier Co-efficient at a junction

A copper-iron junction is immersed in a calorimeter containing water. The Cu-Fe junction is joined to a battery, a rheostat, ammeter and a commutator (Fig. 8.6). A current of i ampere, measured by an ammeter A , is passed for t second. The resulting rise in temperature of water in the calorimeter is noted. Let R be the resistance of the junction. If H_1 joules is the heat produced, then

$$H_1 = i^2 Rt + \pi it \quad \dots(1)$$

The same current is now passed for the same time in the reverse direction. The rise of temperature is again noted. Let H_2 joules be the heat produced. Then,

$$H_2 = i^2 Rt - \pi it \quad \dots(2)$$

From Eqs. (1) and (2), we have

$$(H_1 - H_2) = 2\pi it$$

or

$$\pi = \frac{(H_1 - H_2)}{2it}$$

Let M be the mass of water in the calorimeter and W the thermal capacity of the calorimeter.

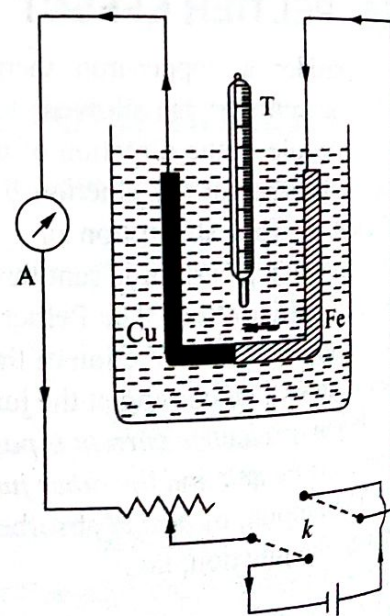


FIG. 8.6

Let θ_1 , and θ_2 be the rises in temperature in the two cases respectively.
Then,

$$H_1 = (M + W) \theta_1 \text{ and } H_2 = (M + W) \theta_2$$

$$(H_1 - H_2) = (M + W) (\theta_1 - \theta_2)$$

$$\pi = \frac{(M + W) (\theta_1 - \theta_2)}{2it}$$

Hence π is determined from the above relation.

Thermodynamical consideration of Peltier Effect

Consider a copper-iron thermocouple with the cold junction at the absolute temperature T_1 and the hot junction at the absolute temperature T_2 (Fig. 8.7). The thermoelectric current i flows in the direction as shown in Fig. 8.7. The flow of this current provides the necessary condition for the Peltier effect to take place and consequently the heat is absorbed at the hot junction and generated at the cold junction. Let π_1 and π_2 be the Peltier coefficients of the cold and the hot junctions respectively.

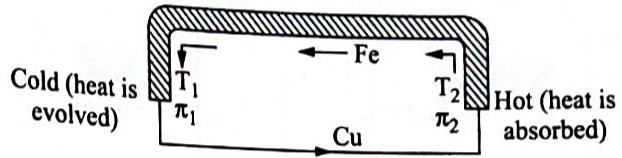


FIG. 8.7

Heat energy absorbed in t seconds at the hot junction = $\pi_2 it$.

Heat energy evolved in t seconds at the cold junction = $\pi_1 it$.

$$\text{Net energy absorbed} = (\pi_2 - \pi_1) it \quad \dots(1)$$

This energy is used in setting up a thermo emf E_p in the circuit.

The electrical energy developed in the thermocouple = $E_p it$.

$$(\pi_2 - \pi_1) it = E_p it$$

$$E_p = (\pi_2 - \pi_1) \quad \dots(2)$$

The thermocouple acts like a heat engine in which an amount of heat energy π_2 is absorbed from the source at a higher temperature T_2 and an amount π_1 is rejected to the sink at the lower temperature T_1 . Applying second law of thermodynamics, we have

$$\frac{\pi_1}{T_1} = \frac{\pi_2}{T_2}, \text{ or } \frac{\pi_2}{\pi_1} = \frac{T_2}{T_1}$$

$$\frac{\pi_2 - \pi_1}{\pi_1} = \frac{T_2 - T_1}{T_1}$$

$$(\pi_2 - \pi_1) = \frac{\pi_1}{T_1} (T_2 - T_1)$$

$$(\pi_2 - \pi_1) \propto (T_2 - T_1) \quad \left(\because \frac{\pi_1}{T_1} \text{ is constant} \right) \quad \dots(3)$$

From Eqs. (2) and (3), we have

$$E_p \propto (T_2 - T_1) \quad \dots(4)$$

Thus the emf developed in the thermocouple is directly proportional to $(T_2 - T_1)$, the temperature difference between the two junctions. The graph between E_p and T should be a straight line.

But it has been found experimentally that the graph between E_p and T is a parabolic curve. This shows that Peltier effect alone cannot explain the thermo-electric phenomenon in a thermocouple. This led to the *discovery of Thomson effect*. Thomson said that there must be some additional source of EMF which has not been taken into account in Peltier effect. *This additional EMF is due to the different parts of the same metal being at different temperatures.* The combined EMF due to the Peltier effect and Thomson effect showed agreement with the experimental results.

8.5 THOMSON EFFECT

Consider a copper bar AB heated in the middle at the point C (Fig. 8.8). A current is passed from A to B . It is observed that heat is absorbed in the part AC and evolved in the part CB . This is known as *Positive Thomson effect*. Similar effect is observed in metals like Ag, Zn, Sb and Cd.

In the case of an iron bar AB , heat is evolved in the part AC and absorbed in the part CB (Fig. 8.9). This is known as *Negative Thomson effect*. Similar effect is observed in metals like Pt, Ni, Co and Bi.

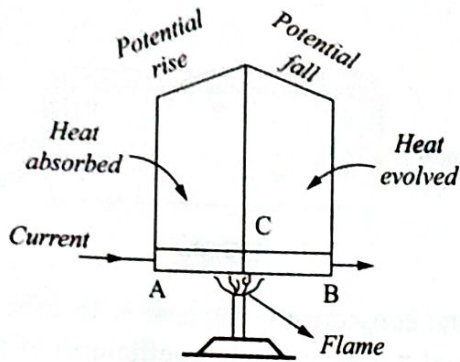


FIG. 8.8

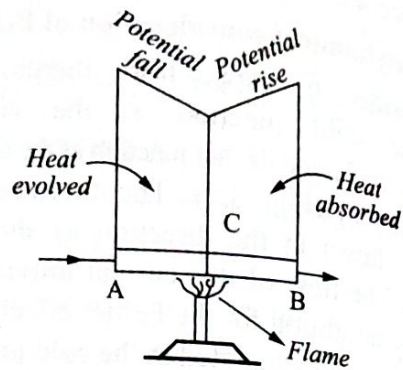


FIG. 8.9

For lead, the Thomson effect is zero.

The Thomson effect is reversible.

In the case of copper, the hotter parts are at a higher potential than the colder ones. It is opposite in the case of iron. Heat is either absorbed or evolved when current passes between two points having a difference of potential. Therefore, the passage of electric current through a metal having temperature gradient results in an absorption or evolution of heat in the body of the metal.

When a current flows through an unequally heated metal, there is an absorption or evolution of heat throughout in the body of the metal. This is known as 'Thomson effect'.

Thomson Coefficient. The Thomson coefficient σ of a metal is defined as the amount of heat energy absorbed or evolved when a charge of 1 coulomb flows in the metal between two points which differ in temperature by 1°C .

Thus, if a charge of q coulomb flows in a metal between two points having a temperature difference of 1°C , then

$$\text{heat energy absorbed or evolved} = \sigma q \text{ joule.}$$

But if E volt be the Thomson emf developed between these points then this energy must be equal to Eq joule.

$$\therefore \sigma q = Eq$$

$$\text{or } \sigma = E.$$

Thus the Thomson coefficient of a metal, expressed in joule per coulomb per $^\circ\text{C}$, is numerically equal to the emf in volt, developed between two points differing in temperature by 1°C .

Hence it may also be expressed in volt per $^\circ\text{C}$.

σ is not a constant for a given metal. It is a function of temperature.

Demonstration of Thomson effect.

Fig. 8.10. shows Starling's method of demonstrating the Thomson effect. An iron rod ABC is bent into U shape. Its ends A and C are dipped in mercury baths. C_1 and C_2 are two insulated copper wires of equal resistance wound round the two

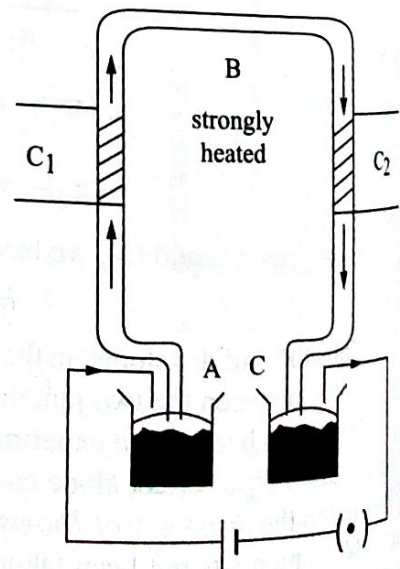


FIG. 8.10

arms of the bent rod. C_1 and C_2 are connected in the opposite gaps of a metre bridge. The bridge is balanced. Then the mid-point B of the rod is strongly heated. A heavy current is passed through the rod. Then this current will be flowing up the temperature gradient in one arm and down the temperature gradient in the other arm. As a result, one of the coils will be cooled and the other will be warmed. The balance in the bridge will be upset and the galvanometer in its circuit will show a deflection. If the direction of the current is reversed, the deflection in the galvanometer will be reversed.

Experimental Determination of Thomson Coefficient.

Fig. 8.11 shows the experimental arrangement for the determination of the absolute value of the Thomson coefficient of a metal at a fixed temperature.

The metal whose Thomson coefficient is to be determined is taken in the form of a wire AB . The wire is stretched in vacuum between two massive leads. These leads are maintained at a selective constant temperature. On passing a steady current through the wire, its temperature is raised due to Joule heating effect. The heating of wire is maximum at its centre since its ends are maintained at the selected constant temperature.

Due to Thomson effect, a cooling effect is produced in one half of the wire whereas a heating effect is produced in the other half. The temperature of the wire at two points H_1 and H_2 , equally distant from its centre O , are measured by a pair of platinum constantan thermocouples. If in addition, the cold junctions are kept at the same temperature as the massive leads, the above determination really represents an excess temperature ϕ .

Let ϕ_1 and ϕ_2 be the excess temperature of points H_1 and H_2 respectively as measured by the thermocouples. We assume that the energy is lost only by conduction along the wire and K denotes the thermal conductivity of its wire. S denotes the cross-section area of the wire. Then, it can be shown that

$$\text{Thomson coefficient, } \sigma = \frac{3\phi_2 KS}{\phi_1 Ib}$$

I is the current in ampere passing through the wire. $OH_1 = OH_2 = b$

If the absolute Thomson coefficient for one metal is known, then its value for all other metals can be determined by the following experimental procedure. A thermocouple is formed between the metal whose Thomson coefficient is desired and whose Thomson coefficient is known. The emf of this thermocouple, measured as a function of temperature with the theoretical Eq.

$$(\sigma_b - \sigma_a) = T \cdot \frac{d^2 E}{dT^2}$$

enables one to determine the difference between the Thomson coefficient for the two metals comprising the thermocouple. Since Thomson coefficient of one of the metals is known, that of other becomes automatically known.

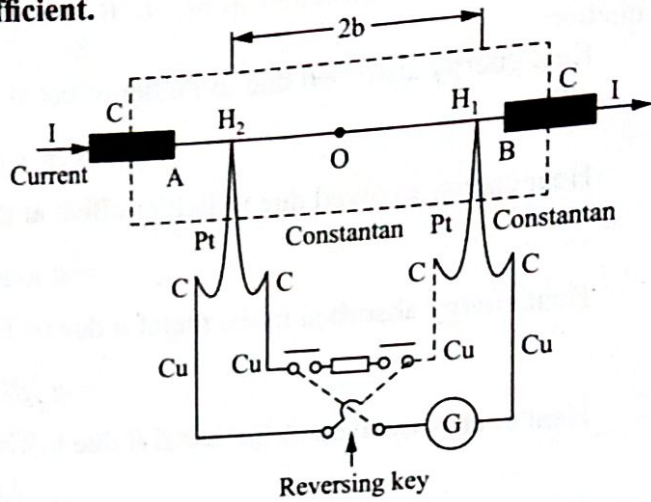


FIG. 8.11

8.6 THERMODYNAMICS OF THERMOCOUPLE (EXPRESSIONS FOR PELTIER AND THOMSON COEFFICIENTS)

Consider a thermocouple consisting of two metals A and B . Let T and $T + dT$ be the temperatures of the cold and hot junctions respectively [Fig. 8.12]. Let π and $\pi + d\pi$ be the Peltier coefficients

for the pair at the cold and hot junctions. Let σ_a and σ_b be the Thomson coefficients for the metals A and B respectively, both taken as positive. When a charge flows through the thermocouple, heat will be absorbed and evolved at the junctions due to Peltier effect and all along the metal due to Thomson effect.

Let 1 coulomb of charge flow through the thermocouple in the direction from A to B at the hot junction.

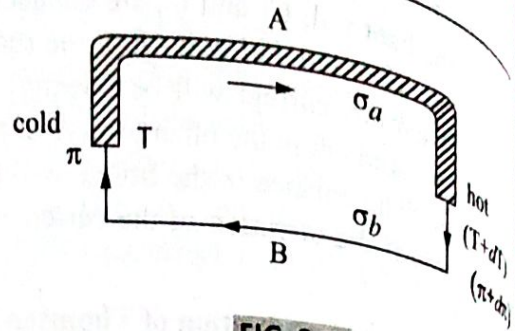


FIG. 8.12

Heat energy absorbed due to Peltier effect at the hot junction

$$= (\pi + d\pi) \text{ joules}$$

Heat energy evolved due to Peltier effect at the cold junction

$$= \pi \text{ joules}$$

Heat energy absorbed in the metal A due to Thomson effect

$$= \sigma_a dT \text{ joules}$$

Heat energy evolved in the metal B due to Thomson effect

$$= \sigma_b dT \text{ joules}$$

\therefore Net heat energy absorbed in the thermocouple

$$= (\pi + d\pi - \pi) + (\sigma_a dT - \sigma_b dT)$$

$$= d\pi + (\sigma_a - \sigma_b) dT$$

This energy is used in establishing a P.D. dE in the thermocouple.

$$\therefore dE = d\pi + (\sigma_a - \sigma_b) dT \quad \dots(1)$$

Since the Peltier and Thomson effects are reversible, the thermocouple acts as a reversible heat engine. Here,

(i) The heat energy $(\pi + d\pi)$ joules is absorbed from the source at $(T + dT)$ K and $\sigma_a dT$ joule is absorbed in metal A at mean temperature T K.

(ii) Also π joule is rejected to sink at T K and $\sigma_b dT$ joule is given out in metal B at the mean temperature T K.

Applying Carnot's theorem, we have

$$\frac{\pi + d\pi}{T + dT} + \frac{\sigma_a dT}{T} = \frac{\pi}{T} + \frac{\sigma_b dT}{T}$$

or

$$\frac{\pi + d\pi}{T + dT} - \frac{\pi}{T} = \frac{(\sigma_b - \sigma_a) dT}{T}$$

or

$$\frac{\pi T + d\pi T - \pi T - \pi dT}{T(T + dT)} = \frac{(\sigma_b - \sigma_a) dT}{T}$$

or

$$d\pi.T - \pi.dT = (\sigma_b - \sigma_a) dT (T + dT)$$

or

$$d\pi.T - \pi dT = (\sigma_b - \sigma_a) T dT + (\sigma_b - \sigma_a) dT^2$$

or

$$(d\pi.T - \pi dT) = (\sigma_b - \sigma_a) T .dT \quad [\text{Neglecting } (\sigma_b - \sigma_a) dT^2]$$

or

$$T[d\pi + (\sigma_a - \sigma_b) dT] = \pi dT$$

But

$$d\pi + (\sigma_a - \sigma_b) dT = dE$$

from Eq. (1)

$$T dE = \pi \cdot dT$$

$$\pi = T \cdot \frac{dE}{dT} \quad \dots(2)$$

The quantity (dE/dT) is called the thermoelectric power (P) .
 Thermoelectric power (P) is defined as the thermo emf per unit difference of temperature between the junctions.

Peltier coefficient = Absolute temperature \times thermoelectric power

Differentiating Eq. (2),

$$\frac{d\pi}{dT} = T \frac{d^2E}{dT^2} + \frac{dE}{dT}$$

Substituting the value of (dE/dT) from Eq. (1),

$$\frac{d\pi}{dT} = T \frac{d^2E}{dT^2} + \frac{d\pi}{dT} + (\sigma_a - \sigma_b)$$

$$(\sigma_a - \sigma_b) = -T \cdot \frac{d^2E}{dT^2}$$

$$(\sigma_b - \sigma_a) = T \cdot \frac{d^2E}{dT^2} \quad \dots(3)$$

If the first metal in the thermocouple is lead, then $\sigma_a = 0$

$$\sigma_b = T \cdot \frac{d^2E}{dT^2} \quad \dots(4)$$

Thomson coefficient = absolute temperature of the cold junction \times first derivative of thermoelectric power.

From Eq. (3),

$$\frac{d^2E}{dT^2} = \frac{(\sigma_b - \sigma_a)}{T} \quad \text{or} \quad \frac{d}{dT} \left(\frac{dE}{dT} \right) = \frac{(\sigma_b - \sigma_a)}{T}$$

Putting dE/dT from Eq. (2), we have

$$\frac{d}{dT} \left(\frac{\pi}{T} \right) = \frac{(\sigma_b - \sigma_a)}{T}$$

$$\frac{d}{dT} \left(\frac{\pi}{T} \right) - \left(\frac{\sigma_b - \sigma_a}{T} \right) = 0 \quad \dots(5)$$

This gives the relation between Peltier and Thomson's coefficients.

Total EMF in a Thermo-couple

Consider a thermo-couple made of two dissimilar metals X and Y (Fig. 8.13). Let the temperatures of the hot and cold junctions be T_1 and T_2 respectively. Let the current be positive from X to Y at the hot junction. Let π_1 and π_2 be the Peltier coefficients at the junctions at T_1 and T_2 respectively. Let σ_x and σ_y be the Thomson coefficients for the metals X and Y respectively. When the electric charge flows in the thermocouple, the heat is absorbed and evolved at the junctions due to Peltier effect and all along the conductor due to Thomson effect. The total emf round the circuit ϵ is the energy gained by unit charge when passing round the circuit.

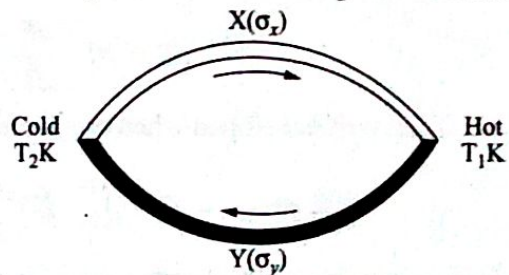


FIG. 8.13

The total emf responsible for the thermocurrent must be the sum of potentials due to Peltier and Thomson effects.

$$\begin{aligned} \epsilon &= \text{Sum of pds. across various parts of the circuit} \\ &= \pi_1 - \pi_2 + \int_{T_2}^{T_1} \sigma_x dT - \int_{T_2}^{T_1} \sigma_y dT \\ &= \pi_1 - \pi_2 + \int_{T_2}^{T_1} (\sigma_x - \sigma_y) dT \end{aligned} \tag{1}$$

It is equal to the total Seebeck emf available in the circuit. Eq. (1) is the expression for the total thermo-emf developed in a thermocouple.

8.7 THERMO-ELECTRIC DIAGRAMS

A thermocouple is formed from two metals *A* and *B*. The difference of temperature of the junctions is *T* K. The thermo emf *E* is given by the equation

$$E = aT + bT^2$$

A graph between *E* and *T* is a parabola.

$$\frac{dE}{dT} = a + 2bT$$

dE/dT is called *thermoelectric power*.

A graph between thermoelectric power (*dE/dT*) and difference of temperature *T* is a straight line. This graph is called the *thermo-electric power line* or the *thermo-electric diagram*. Thomson coefficient of lead is zero. So generally thermoelectric lines are drawn with lead as one metal of the thermocouple. The thermoelectric line of a Cu-Pb couple has a positive slope while that of Fe-Pb couple has a negative slope. Fig. 8.14 shows the power lines for a number of metals.

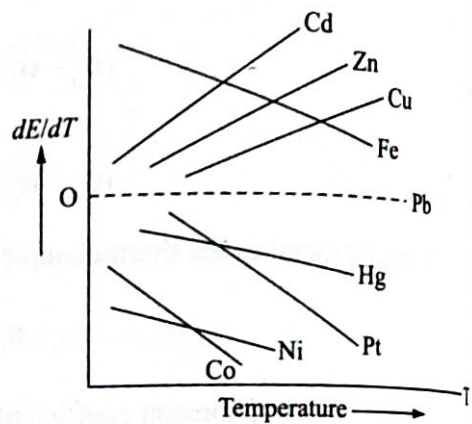


FIG. 8.14

Uses of Thermoelectric Diagrams

(i) **Determination of Total emf.** *MN* represents the thermo-electric power line of a metal like copper coupled with lead (Fig. 8.15). *MN* has a positive slope. Let *A* and *B* be two points corresponding to temperatures *T*₁ K and *T*₂ K respectively along the temperature-axis. Consider a small strip *abdc* of thickness *dT* with junctions maintained at temperatures *T* and (*T* + *dT*).

The emf developed when the two junctions of the thermocouple differ by *dT* is

$$dE = dT \left(\frac{dE}{dT} \right) = \text{area } abdc$$

Total emf developed when the junctions of the couple are at temperatures *T*₁ and *T*₂ is

$$E_s = \int_{T_1}^{T_2} dT \left(\frac{dE}{dT} \right) = \text{Area } ABDC$$

(ii) **Determination of Peltier emf.** Let *π*₁ and *π*₂ be the Peltier coefficients for the junctions of the couple at temperatures *T*₁ and *T*₂ respectively.

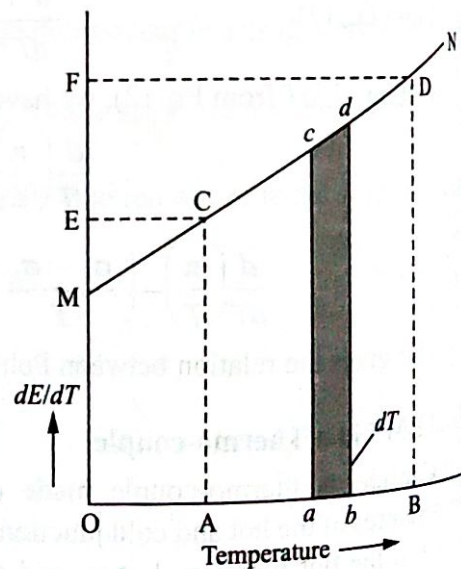


FIG. 8.15

The Peltier coefficient at the hot junction (T_2) is

$$\pi_2 = T_2 \left(\frac{dE}{dT} \right)_{T_2} = OB \times BD = \text{area } O B D F$$

Similarly, Peltier coefficient at the cold junction (T_1) is

$$\pi_1 = T_1 \left(\frac{dE}{dT} \right)_{T_1} = OA \times AC = \text{area } O A C E$$

π_1 and π_2 give the Peltier emfs at T_1 and T_2 respectively. Peltier emf between temperatures T_1 and T_2 is

$$E_p = \pi_2 - \pi_1 = \text{area } O B D F - \text{area } O A C E = \text{area } A B D F E C A$$

(iii) **Determination of Thomson emf.** Total emf developed in a thermocouple between temperatures T_1 and T_2 is

$$\therefore E_s = (\pi_2 - \pi_1) + \int_{T_1}^{T_2} (\sigma_a - \sigma_b) dT$$

Here σ_a and σ_b represent the Thomson coefficients of two metals constituting the thermocouple. If the metal A is copper and B is lead, then $\sigma_b = 0$.

$$\therefore E_s = (\pi_2 - \pi_1) + \int_{T_1}^{T_2} (\sigma_a dT)$$

$$\text{or} \quad \int_{T_1}^{T_2} \sigma_a dT = -[(\pi_2 - \pi_1) - E_s]$$

Thus, the magnitude of Thomson emf is given by

$$E_{th} = (\pi_2 - \pi_1) - E_s = \text{Area } A B D F E C A - \text{Area } A B D C \\ = \text{Area } C D F E$$

(iv) **Thermo emf in a general couple, neutral temperature and temperature of inversion.** In practice, a thermocouple may consist of any two metals. One of them need not be always lead. Let us consider a thermocouple consisting of any two metals, say Cu and Fe . AB and CD are the thermo-electric power lines for Cu and Fe with respect to lead (Fig. 8.16). Let T_1 and T_2 be the temperatures of the cold and hot junctions corresponding to points P and Q .

$$\text{Emf of } Cu - Pb \text{ thermocouple} = \text{Area } P Q B_1 A_1$$

$$\text{Emf of } Fe - Pb \text{ thermocouple} = \text{Area } P Q D_1 C_1$$

\therefore the emf of $Cu - Fe$ thermocouple is

$$E_{Cu}^{Fe} = \text{Area } P Q D_1 C_1 - \text{Area } P Q B_1 A_1 - \text{Area } A_1 B_1 D_1 C_1$$

The emf E_{Cu}^{Fe} increases as the temperature of the hot junction is raised and becomes maximum at the temperature T_n , where the two thermoelectric power lines intersect each other. The temperature T_n is called the neutral temperature. As the thermo emf becomes maximum at the neutral temperature, at $T = T_n, (dE/dT) = 0$.

Suppose temperatures of the junctions, T_1 and T_2 , for a $Cu - Fe$ thermocouple are such that the neutral temperature T_n lies between T_1 and T_2 (Fig. 8.17). Then the thermo emf will

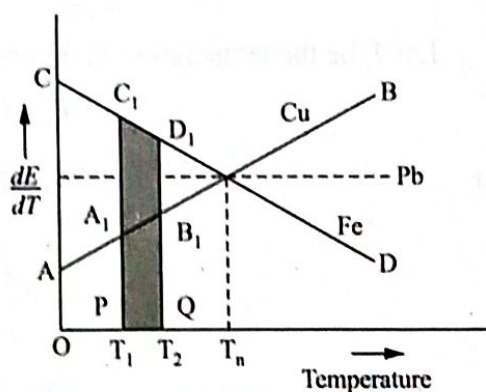


FIG. 8.16

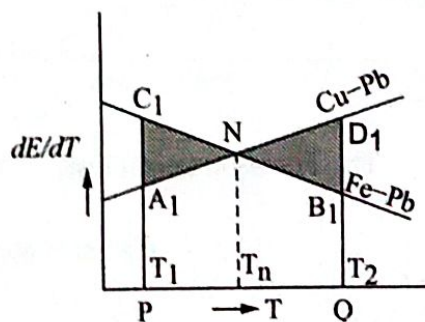


FIG. 8.17

be represented by the difference between the areas A_1NC_1 and B_1D_1N because these areas represent opposing emf's. In the particular case when $T_n = (T_1 + T_2)/2$, these areas are equal and the resultant emf is zero. In this case, T_2 is the 'temperature of inversion' for the Cu-Fe thermocouple.

Example 1. The emf of a thermocouple, one junction of which is kept at 0°C , is given by $E = at + bt^2$. Determine the neutral temperature, temperature of inversion and the Peltier and Thomson coefficients.

Solution. $E = at + bt^2$

Now,

$$t^\circ\text{C} = (T - 273)^\circ\text{C}, \text{ where } T \text{ is in absolute degrees.}$$

\therefore

$$E = a(T - 273) + b(T - 273)^2$$

$$\text{Differentiating, } \frac{dE}{dT} = a + 2b(T - 273)$$

and

$$\frac{d^2E}{dT^2} = 2b.$$

At the neutral temperature, $T = T_n$ and $\frac{dE}{dT} = 0$

\therefore

$$0 = a + 2b(T_n - 273)$$

or

$$T_n - 273 = -\frac{a}{2b}$$

or

$$T_n = \left(273 - \frac{a}{2b}\right) \text{K} = \left(-\frac{a}{2b}\right)^\circ\text{C}$$

Let T_i be the temperature of inversion. Then,

$$T_n = (273 + T_i)/2$$

or

$$T_i = 2T_n - 273 = 2\left(273 - \frac{a}{2b}\right) - 273$$

$$= \left(273 - \frac{a}{b}\right) \text{K} = -\left(\frac{a}{b}\right)^\circ\text{C}$$

The Peltier coefficient, $\pi = T \frac{dE}{dT}$

$$= T[a + 2b(T - 273)]$$

$$= (t + 273)(a + 2bt)$$

The Thomson coefficient, $\sigma = T \frac{d^2E}{dT^2}$

$$= T \cdot 2b$$

$$= 2b \cdot (t + 273)$$

Example 2. A thermo-couple is made of iron and constantan. Find the emf developed per $^\circ\text{C}$ difference of temperatures between the junctions, given that thermo-emfs of iron and constantan against platinum are $+1600$ and $-3400 \mu\text{V}$ per 100°C difference of temperatures.

Solution. According to the law of intermediate metals,

$$E_{con}^{Fe} = E_{Pt}^{Fe} + E_{con}^{Pt} = E_{Pt}^{Fe} - E_{Pt}^{con}$$

Now,

$$E_{Pt}^{Fe} = 1600 \mu V/100^\circ C = 16 \mu V/^\circ C$$

and

$$E_{Pt}^{con} = -3400 \mu V/100^\circ C = -34 \mu V/^\circ C$$

∴

$$E_{con}^{Fe} = 16 - (-34) = 50 \mu V/^\circ C$$

3. The thermo-electric power of iron is $17.3 \mu V/^\circ C$ at $0^\circ C$ and $12.5 \mu V/^\circ C$ at $100^\circ C$ and that for silver $2.9 \mu V/^\circ C$ and $4.1 \mu V/^\circ C$ at the same two temperatures. Calculate

- (1) Peltier co-efficient between iron and silver at $100^\circ C$.
- (2) Thomson co-efficient of iron at $50^\circ C$.
- (3) Thermo e.m.f. when the two junctions are at $0^\circ C$ and $100^\circ C$.
- (4) Neutral temperature of the couple formed by the 2 metals.
- (5) Temperature of inversion when the cold junction is at $50^\circ C$.

Solution. (1) Thermoelectric power between the metals at $100^\circ C$

$$= 12.5 - 4.1 = 8.4 \mu V/^\circ C$$

$$\left. \begin{array}{l} \text{Peltier emf} \\ \text{at } 100^\circ C \end{array} \right\} = T \frac{dE}{dT} = 373 \times 8.4 = 3133 \mu V$$

Peltier coefficient = $3.133 \times 10^{-3} J/C$

(2) Slope of the thermoelectric diagram

$$= \frac{d}{dT} \left(\frac{dE}{dT} \right) = \frac{12.5 - 17.3}{100} = -\frac{4.8}{100} = -0.048 \mu V/^\circ C$$

Thomson coefficient σ at $50^\circ C$

$$= T \frac{d^2 E}{dT^2} = -323 \times 0.048 \times 10^{-6} = -15.5 \times 10^{-6} K^{-1}$$

(3) Thermo emf = area of trapezium ABCD (Fig. 8.18)

$$= \frac{1}{2} \times (14.4 + 8.4) 100$$

$$= 1140 \mu V$$

$$(4) \frac{17.3 - 2.9}{T_n} = \frac{12.5 - 4.1}{T_n - 100}$$

$$\frac{14.4}{T_n} = \frac{8.4}{T_n - 100}$$

$$T_n = 240^\circ C$$

or

(5) If T_i is the temperature of inversion when the cold junction is at $50^\circ C$,

$$\frac{T_i + 50}{2} = T_n = 240$$

$$T_i + 50 = 480$$

$$T_i = 430^\circ C$$

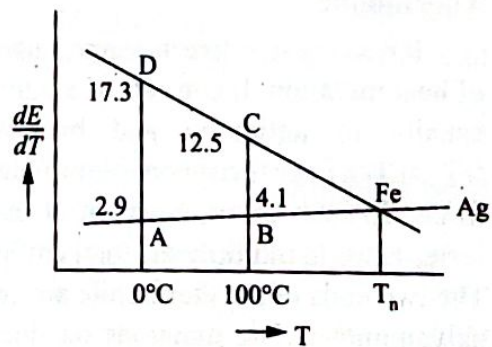


FIG. 8.18

8.8 APPLICATIONS OF THERMO-ELECTRICITY

Boys Radio-micrometer

Construction. It is a combination of a moving coil galvanometer and a thermocouple. It consists of a single loop of silver wire *A* to the lower end of which two strips of antimony and bismuth are attached (Fig.8.19). The lower ends of these strips are soldered to a copper disc coated with lamp black. The loop of wire is suspended between the pole-pieces of a powerful magnet with the help of a quartz fibre which also carries a small mirror *M*.

Working. When heat radiation falls on the disc, thermoelectric current is produced in Sb-Bi thermocouple and the current flows through the silver wire *A*. The deflection produced in the galvanometer can be measured with a lamp and scale arrangement. This instrument is very sensitive to detect heat radiations.

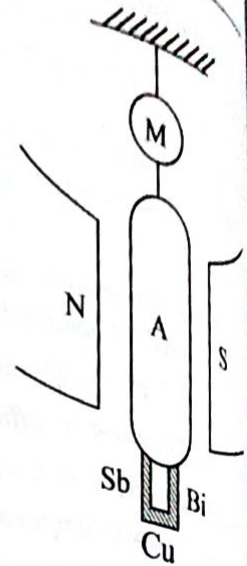


FIG. 8.19

Thermo-electric Pyrometer

Pyrometer is an instrument used to measure very high temperatures such as the temperature of a furnace. It works on the principle of thermo electric effect.

A thermocouple of Pt and an alloy of Pt-iridium is used. Two long wires of these two materials are threaded through fine porcelain tubes and their ends fused together at the bottom (Fig. 8.20). This arrangement is placed in an outer porcelain tube having two terminals at the top. A moving coil galvanometer can be connected to these two terminals. The thermoelectric current produced can be detected by the galvanometer and the galvanometer scale is calibrated. Pyrometers are commonly used to check any variation in the temperature of furnaces in Thermo-electric Pyrometer metallurgy.

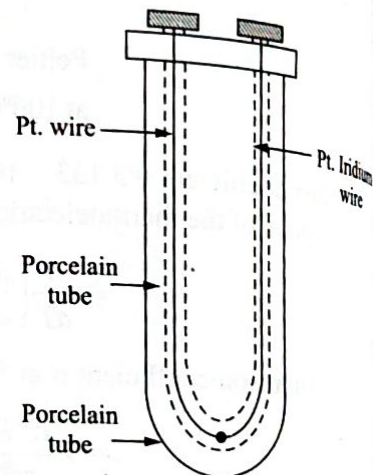


FIG. 8.20

Thermopile

It is a very sensitive instrument used to detect the presence of heat radiation. It consists of a number of thermocouples, usually of antimony and bismuth, joined in series (Fig. 8.21). Each thermocouple produces some electromotive force. So such an arrangement of thermocouples joined in series helps to multiply the total emf produced in the circuit. The two ends of the thermopile are connected to a sensitive galvanometer. The junctions on one side are coated with lampblack and are exposed to heat radiations. The junctions on the other side are kept cold. The deflection in the galvanometer measures the intensity of heat radiations and the scale can be calibrated.

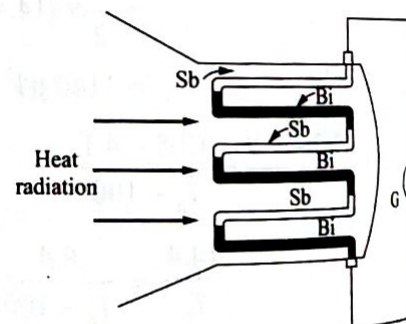


FIG. 8.21

EXERCISE

1. Explain Seebeck effect. Describe the laws of thermoelectric effects.
2. Describe a method of measuring the thermo emf.

3. What is meant by Peltier effect? How would you demonstrate it experimentally? How does it differ from Joule heating effect? Define Peltier coefficient.
4. Explain Thomson effect. Define Thomson coefficient. Describe an experiment to demonstrate Thomson effect.
5. Prove that the Peltier coefficient of a pair of metals is the product of the absolute temperature and thermoelectric power.
6. Applying thermo-dynamic considerations to the working of a thermo-couple show that

$$\pi = T \cdot \frac{dE}{dT} \text{ and } \sigma_a - \sigma_b = -T \cdot \frac{d^2E}{dT^2}$$

where the symbols have their usual meaning.

7. What is a thermo-electric diagram? Show how Peltier and Thomson e.m.f.'s, neutral temperature and the temperature of inversion can all be represented in this diagram.
8. The emf (micro volts) in a lead-iron thermocouple, one junction of which is at 0°C is given by $E = 1784t - 2.4t^2$ where t is the temperature in degree centigrade. Find the neutral temperature and Peltier and Thomson coefficients.
9. If for a certain thermo-couple $E = at + bt^2$ where $t^\circ\text{C}$ is the temperature of the hot junction, the cold junction being at 0°C , $a = 10$ microvolt/ $^\circ\text{C}$, $b = -1/40$ microvolt/ $^\circ\text{C}^2$, find the neutral temperature and the temperature of inversion.
10. Thermo emf in a circuit in which the cold junction is at 0°C and the hot junction at $t^\circ\text{C}$ is found to be $3.5 \mu\text{V}$ at 100°C and $9 \mu\text{V}$ at 200°C . Assuming the thermo emf to be governed by the equation $E = at + bt^2$, find the constants a and b .

Hint. $3.5 \times 10^{-6} = a \times 100 + b \times 100^2$;

$$9 \times 10^{-6} = a \times 200 + b \times 200^2.$$

Solving, $a = 3.51 \times 10^{-8} \mu\text{V}/^\circ\text{C}$; $b = -10^{-10} \mu\text{V}/^\circ\text{C}^2$.

11. The thermo-electric power of iron is 17.5 microvolt per degree at 0°C and zero at 360°C ; that of copper is 5 microvolts per degree at 450°C and zero at -50°C . Find the value of the e.m.f. of a copper-iron couple when the cold junction is at 0°C and the hot junction at the neutral temperature (Assume the thermo-electric lines to be straight).
12. Find the thermo e.m.f generated in a thermocouple, when its junctions are kept at 160°C and 50°C respectively, if e.m.fs generated in the thermo-couple, when its hot junctions are at 160°C and 50°C are 25 microvolts and 5.6 microvolts respectively. (The temperature of the cold junction being 0°C).

ANSWERS

8. 371.7°C , $T(1784 - 4.8 t)$, $-4.8 T$
9. 200°C , 400°C
11. 2465 micro-volts
12. $19.4 \mu\text{V}$